

## Sample Exam – Power Systems -- 2021

This **sample exam** is intended to provide an indication of the type, style and complexity of questions in the official exam in November 2021. The topics covered in this sample should **NOT** be used as an indication of the topics to be covered in the official exam. That is, revision should include all course material including lectures, tutorials, quizzes, sample quizzes and assignments and should not be restricted to the topics covered in this sample exam.

This sample exam is for both the undergraduate and postgraduate versions of the course. The distinction is that postgraduates will be required to answer all five questions in the allotted time of 150 min whereas undergraduates will be required to answer the first four questions in the allotted time of 120 min.

### Question 1. Sinusoids, phasors and ac circuits [ 20 marks ]

### 1a) Sinusoidal Waveforms and Phasors [ 8 marks ]

A balanced 50 Hz sinusoidal three-phase voltage source with phase sequence abc supplies a balanced three-phase system. The phase 'a' to neutral voltage is represented by an anti-clockwise-rotating, cosine-referenced, RMS, phasor

$$\hat{V}_{an} = 158.8e^{-j(\pi/12)} \text{ kV} \quad (1)$$


and the phase ‘a’ line current is represented by the phasor of the same type

$$\hat{I}_a = 210 \angle -30^\circ \text{ A} \quad (2)$$

- i) Express the voltage as a sinusoidal function of time. [ 2 marks ]
  
  
  
  
  
  
  
  
  
  
- ii) Clearly sketch the voltage waveform from time  $t = 0$  marking clearly the value of the voltage at  $t = 0$  and the times and values of the first minimum and maximum voltage. [ 3 marks ]
  
  
  
  
  
  
  
  
  
  
- i) Calculate the three-phase real power ( $P$ ) and reactive power ( $Q$ ) generated by the source. [ 3 marks ]

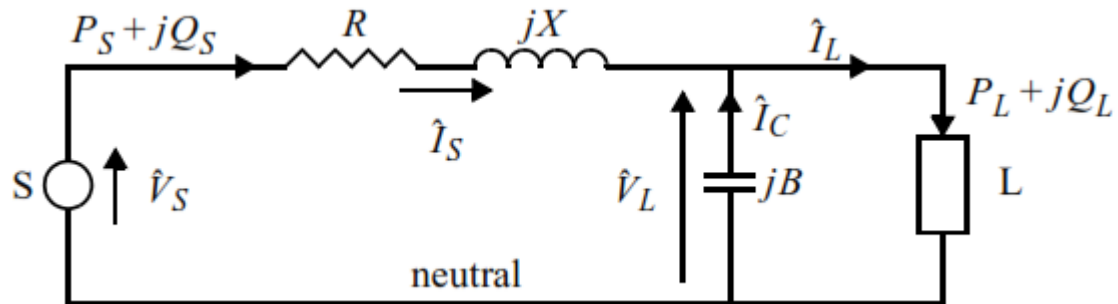**1b) Circuit Analysis [ 12 marks ]**

Consider the following circuit showing a single phase of a balanced three-phase network. The network parameters are in per-unit on a three-phase MVA base of 100 MVA and voltage base of 275 kV (rms, l-l).



Parameter	Value (per-unit on 100 MVA, 275 kV (rms, l-l))
R (resistance)	0.05
X (reactance)	0.15
B (susceptance)	0.50

**1b)(I) Circuit Analysis (Part I) [ 6 marks ]**

The load bus voltage phasor is  $\hat{V}_L = 1.05 \angle 0^\circ$  pu and the load is  $P_L + jQ_L = 120 + j40$  MW/MVAr.

- Calculate the current phasor  $\hat{I}_C$  in per-unit. [ 1 mark ]
- Calculate the reactive power generated by the shunt capacitance in per-unit and MVAr? [ 1 mark ]
- Calculate the per-unit load current phasor  $(\hat{I}_L)$ ? [ 2 marks ]

- iv) Calculate the per-unit source current phasor  $(\hat{I}_S)$ ? [ 2 marks ]

**1b)(II) Circuit Analysis (Part II) [ 6 marks ]**

For a different operating condition than that in 1b(I) the load bus voltage phasor is found to be

$\hat{V}_L = 0.98\angle 0^\circ$  pu and the source current is  $\hat{I}_S = 1.4 - j0.4$  pu.

- i) Calculate the real power loss in transmitting the power from the source to the load in per-unit and MW? [ 1 mark ]
- ii) Calculate the per-unit source voltage phasor  $(\hat{V}_S)$  magnitude and phase angle? [ 2 marks ]
- iii) Calculate the real and reactive power  $(P_S + jQ_S)$  supplied by the source in per-unit and in MW / MVar? [ 3 marks ]


## Question 2. Power System Analysis [ 20 marks ]

### 2a) Derivation of complex power transmission equations [ 6 marks ]

In the loss-less transmission system shown in the following figure recall that:

$$P_S = P_R = \left( \frac{V_S V_R}{X} \right) \sin(\delta), \quad Q_S = \frac{V_S^2}{X} - \left( \frac{V_S V_R}{X} \right) \cos(\delta), \quad Q_R = \left( \frac{V_S V_R}{X} \right) \cos(\delta) - \frac{V_R^2}{X}$$

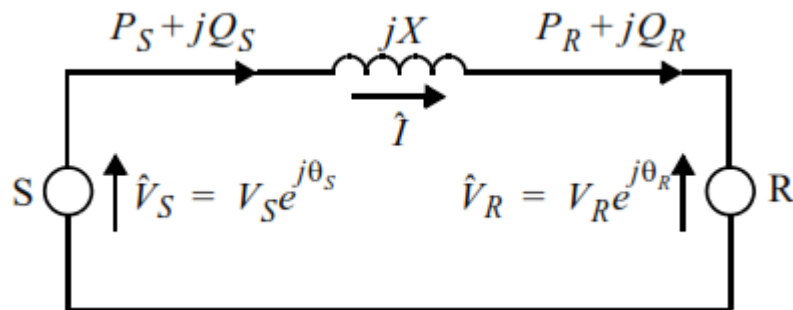
in which  $\delta = \theta_S - \theta_R$  is the transmission angle.



Referring to **Error! Reference source not found.** derive the equations for the real and reactive power delivered to the receiving end (R) (i.e.  $P_R$  and  $Q_R$  in equation **Error! Reference source not found.**). You must clearly show the steps in your derivation.
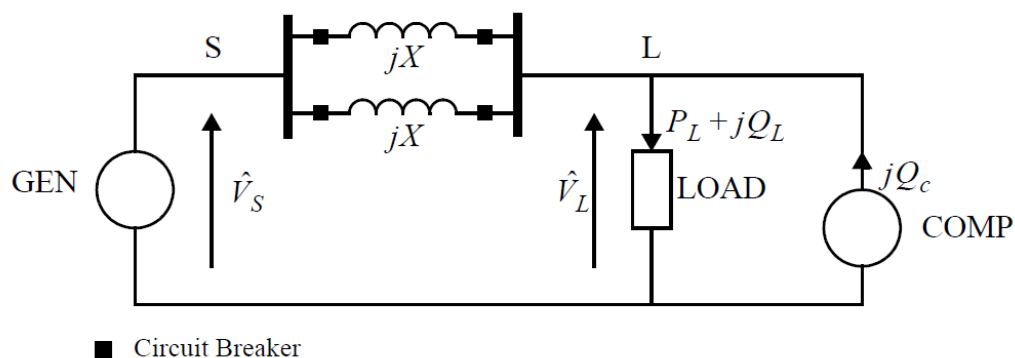
## 2b) Reactive power compensation and voltage control [ 14 marks ]

Consider the network in the following figure in which two identical transmission lines, each with reactance  $X = 0.3$  pu, supply a load from a generating source connected to node S. A static VAR compensator (SVC) is connected to the load bus, L, to control the load bus voltage to a specified value.



The maximum load to be securely supplied by the network is  $P_{L\max} = 2.0$  pu at a power factor of 0.95 (lag) and the source voltage magnitude is  $V_S = 1.05$  pu. The compensator is required to control the load bus voltage to  $V_L = 1.05$  pu.

- a) For the purpose of determining the required reactive power capacity of the SVC do you assume that there are one or two transmission lines operating? Explain why. [ 2 marks ]

- b) Calculate the minimum reactive power capacity of the SVC required to securely supply the load. [ 6 marks ]

- c) Give two reasons for conducting power-flow analysis of power systems. [ 2 marks ]

- d) Explain why it is not possible to transmit reactive power long distances in a power system.  
[ 2 marks ]

- e) If it is necessary to increase the voltage at a network bus would you connect a capacitor or inductor? Explain why.  
[ 2 marks ]



**Question 3. Frequency and power control [ 20 marks ]****3a) Steady-state governor droop characteristic [ 4 marks ]**

A generating unit with a power rating of 250 MW is operating steadily at synchronous speed with a power output of 200 MW. The steady-state governor droop is 0.06 per-unit on the power rating of the unit. Sketch the per-unit governor steady-state characteristic representing this operating condition. Mark clearly on the characteristic the value of the generator rotor speed when the power output is (a) zero; and (b) one per-unit.

**3b) Parallel operation of generating units [ 9 marks ]**

Two generators are operating in parallel to supply an isolated load. The generators are fitted with governors with a steady-state droop characteristic. The power ratings and droop settings of the generators are listed in the following table.

Gen	Power Rating (MW)	Governor Steady-State Droop (pu on generator power rating)
1	500	0.03
2	800	0.05

The system load is frequency dependent and is found to increase by 1.5% due to a frequency increase of 1%. Initially the network frequency is 50 Hz and generators 1 & 2 are supplying 350 MW and 500 MW respectively. The load is increased abruptly by 30 MW (as determined at 50 Hz) from 850 to 880 MW. Calculate the resulting steady-state change in frequency (in Hz), and the steady-state changes in the power output of each of the two generating units (in MW).



**3d) Load and frequency control of interconnected power systems**  
**[ 7 marks ]**

- i) A test is conducted on a 50 Hz system to determine its frequency “stiffness”. Immediately before the test the system frequency is 50 Hz and the Automatic Generation Control (AGC) is disabled temporarily. A load of 400 MW is connected to the system. It is found that the system frequency settles to a value of 49.95 Hz. What is the frequency stiffness of the system in MW / Hz? [ 2 marks ]
- ii) Explain why isochronous (i.e. constant speed) governors cannot be used to control frequency when two or more generators are connected in parallel. [ 2 marks ]
- iii) Summarize the purpose of the primary, secondary and tertiary power / frequency controls of a power system. [ 3 marks ]

## Question 4. Power-flow analysis and fault calculations [ 20 marks ]


### 4a) Transmission Lines [ 7 marks ]

Consider a 500 kV (rms, l-l) transmission line of length 250 km connected between constant voltage sources at the sending (S) and receiving (R) ends of the line. The line is assumed to be lossless and with an inductance of  $L = 0.862 \times 10^{-3}$  H / phase / km and capacitance of

$C = 13.79 \times 10^{-9}$  F / phase / km . The system frequency is 50 Hz. The magnitude of the voltage at each end of the line is 525 kV (rms l-l) and the voltage source at the receiving end of the line is absorbing 2000 MW of power from the line at unity power factor. Calculate the reactive power supplied to the sending end of the line.

**4b) Voltage control with transformer taps [ 4 marks ]**


The generator step-up transformer in the following circuit has a leakage reactance of  $x_T = 0.15$  pu on the transformer MVA rating of 500 MVA. The generator is supplying 350 MW at a lagging power factor of 0.97 and its automatic voltage regulator is regulating its terminal voltage to  $|\hat{V}_G| = 1.0$  pu.

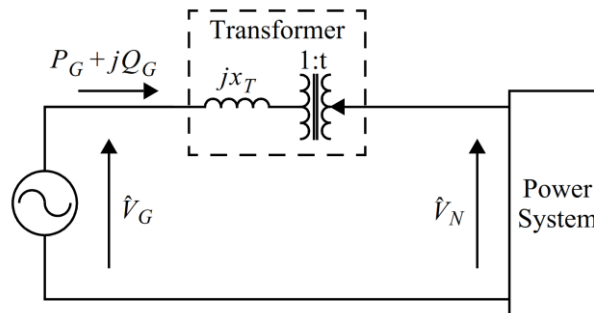

Calculate the tap position  $t$  such that the magnitude of the network voltage  $|\hat{V}_N| = 1.05$  pu.

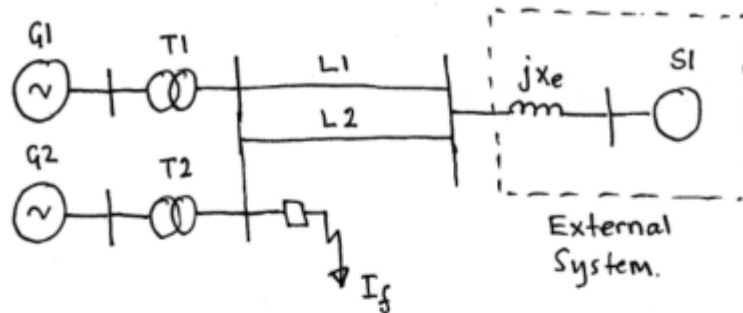**4c) Fault current calculation. [ 8 marks ]**

Consider the following power system one-line diagram.



Item	Parameters
G1	Two identical units each with $X_d'' = 0.25$ pu on 250 MVA, 16 kV
T1	Two identical units each with $X_t = 0.12$ pu on 280 MVA, 16 / 275 kV
G2	$X_d'' = 0.2$ pu on 500 MVA, 24 kV
T2	$X_t = 0.15$ pu on 600 MVA, 24 / 275 kV
L1	275 kV, 200 km line with $R = 0.04$ ohm / ph / km; $X_L = 0.319$ ohm / ph / km and $B_C = 3.651 \times 10^{-6}$ S / ph / km.
L2	Identical to line L1.
Xe	0.008 pu on 100 MVA, 275 kV
S1	Ideal source (no internal impedance)


- i) Draw the network diagram to be used for the purpose of calculating balanced three phase fault currents. Show all network impedances in per-unit on 100 MVA. [ 4 marks ]

- ii) Calculate the fault current  $I_f$  in per-unit due to a balanced three phase fault as indicated in the power-circuit one-line diagram. [ 4 marks ]

## Question 5. Powerflow limits and short answer questions [ 20 marks ]
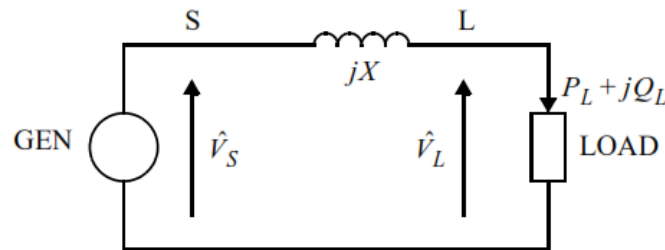
### 5a) Powerflow limits [ 10 marks ]

Consider the following circuit in which all quantities are in per-unit on a consistent set of base values.



Quantity	Value (per-unit)
$X$	0.3
$V_S =  \hat{V}_S $	1.0

- i) If the reactive power consumed by the load ( $Q_L$ ) is zero, calculate the load power ( $P_L$ ) at which the load bus voltage ( $V_L$ ) is 0.9 pu. [ 3 marks ]

- ii) Calculate the maximum load that can be supplied at unity power factor. [ 7 marks ]





**5c) Short answer questions [ 10 marks ]**

Answer the following questions using words only (that is, without any sketches, drawings or equations).

- i) Summarize the mission of a power system. [ 3 marks ]
- ii) Briefly describe how the voltage of a power system is controlled. [ 3 marks ]
- iii) Explain the significance of the surge impedance load of a transmission line. [ 2 marks ]

- iv) Explain the purpose of power system stabilizers fitted to synchronous generators.  
[ 2 marks ]